

Shahjalal University of Science and Technology
Department of Computer Science and Engineering
2nd Year 2nd Semester Final Examination-2022 (Session: 2020-21)
Course Code: EEE 201D Credit: 3.0
Course Title: Digital Logic Design
Time: 3 hours Total Marks: 100

Group – A

1. Answer any FIVE of the following:

5x2=10

- Using block diagram briefly explain how sequential circuits differ from combinational circuits.
- Describe why DRAMs are called dynamic RAM.
- Show that a positive logic NAND gate is a negative logic NOR gate and vice versa.
- Define multiplexers. Also, draw the two-to-one line multiplexer using only AND, OR and inverter gate.
- Using minimum number of NAND gates, implement XOR gate.
- Express the following function as a sum of minterms:

$$F(A, B, C, D) = B'D + A'D + BD$$

- Obtain a truth table for the following function: $F(x, y, z) = (xy + z)(y + xz)$.
- Find the Boolean expression for the logic circuit in figure 1.1.

 


Figure: 1.1

2. Answer any FOUR questions of the following:

4x5=20

- Implement a 32x1 multiplexer using 8x1 multiplexer. You may use basic gates if necessary.
- Design and implement a binary full subtractor.
- Draw block diagram of a four-bit binary ripple carry adder and explain its working principle.
- Simplify the following Boolean function to minimized SOP and POS from-

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15) + \sum_d(0, 2, 5)$$

- Simplify the following functions and implement them with two-level NOR gate circuits:

$$1. F = wx' + y'z' + w'yz'$$

$$2. F = (w, x, y, z) = \Sigma(0, 3, 12, 15)$$

- Implement J-K flip-flop using D flip-flop.

3. Answer any TWO questions of the following:

2x10=20

- In excess-3 code, numbers are represented as decimal digits, and each digit is represented by four bits as the digit value plus 3. i) Make a truth table for a BCD to excess-3 converter, ii) Find the Boolean expressions in minimized SOP form, ii) implement the logic circuit using minimum number of basic gates.
- Implement a full adder with two 4x1 multiplexers
- Design a four-input priority encoder with input D_0 having the highest priority and input D_3 the lowest priority.

Group – B

4. Answer any FIVE questions of the following:

5x2=10

- Define decoder and encoder.
- Explain the differences between a truth table, a state table, a characteristic table and an excitation table
- Differentiate between serial mode and parallel transfer mode of register.
- Briefly explain your understanding on excitation table.
- Write the characteristic and excitation table of a T flip-flop.
- A memory unit is specified by $1G \times 32$. Find how many address lines, input lines, output lines are required. Also find the capacity of the memory.

- g. What is a register? Draw the logic diagram of a four-bit register
 h. Determine the Q output waveform if the inputs shown in Figure: 4.1 are applied to a gated S-R latch that is initially RESET.

 


Figure: 4.1

5. Answer any FOUR questions of the following
- Using proper block diagram, explain the differences among combinational programmable logic devices.
 - Draw logic circuit of a bi-directional shift register and briefly explain its operation.
 - From the state diagram, obtain the logic diagram of BCD ripple counter.
 - Draw logic diagram and timing diagram of Johnson counter. Briefly describe its operation.
 - Draw logic circuit of master-slave J-K flip-flop and briefly explain its operation.
 - Reduce the state diagram shown in figure 4.2 and draw the reduced diagram.

4x5=20

 


Figure: 4.2

6. Answer any TWO questions of the following:
- Tabulate the truth table for an 8 * 4 ROM that implements the following Boolean functions-

2x10=20

$$A(x, y, z) = \sum(0, 3, 4, 6)$$

$$B(x, y, z) = \sum(0, 1, 4, 7)$$

$$C(x, y, z) = \sum(1, 5)$$

$$D(x, y, z) = \sum(0, 1, 3, 5, 7)$$

Draw the fusing map of the ROM logic circuit. Considering now the ROM as a memory, specify the memory contents at addresses 1 and 4.

- Implement the following Boolean function F, together with the don't-care conditions d, using no more than two NOR gates:

$$F(A, B, C, D) = \sum(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \sum(0, 1, 5, 8)$$

Draw the fusing map of the ROM logic circuit. Considering now the ROM as a memory, specify the memory contents at addresses 1 and 4.

- Tabulate the PLA programming table for the four Boolean functions listed below. Minimize the number of product terms. Mark the fuse map in PLA diagram.

$$A(x, y, z) = \sum(1, 3, 5, 6)$$

$$B(x, y, z) = \sum(0, 1, 6, 7)$$

$$C(x, y, z) = \sum(3, 5)$$

$$D(x, y, z) = \sum(1, 2, 4, 5, 7)$$